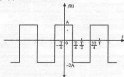


1. (C) The eigen values of a skew-symmetric matrix are either zero or pure imaginary.

2. (C) $f(t) = \text{even function for all } t$



$$f(t) = \begin{cases} A & -\frac{T}{4} < t < \frac{T}{4} \\ -2A & \frac{T}{4} < t < \frac{3T}{4} \\ A & \frac{3T}{4} < t < T \end{cases}$$

$$\begin{aligned} \text{DC term} &= \frac{1}{T} \left[\int_{-3A}^{3A} f(t) dt + \int_{3A}^{3T/4} f(t) dt + \int_{3T/4}^T f(t) dt \right] \\ &= \frac{1}{T} \left[\int_{-3A}^{3A} A dt + \int_{3A}^{3T/4} -2A dt + \int_{3T/4}^T A dt \right] \\ &= \frac{1}{T} \left[A \cdot \frac{T}{2} - 2A \cdot \frac{T}{2} + A \cdot \frac{T}{4} \right] \\ &= \left[\frac{A}{2} - A + \frac{A}{4} \right] \\ &= \frac{3A}{4} - \frac{4A}{4} = -\frac{A}{4} \quad (-ve) \end{aligned}$$

$$a_n = \frac{1}{T} \int f(t) \sin n\omega t dt = 0$$

$$b_n = \frac{2 \times 1}{T} \int_0^T f(t) \cos n\omega t dt = 0$$

Hence, only cosine terms and negative value for the d.c. component.

3. (D) $\frac{d^2 r(x)}{dx^2} - \frac{r(x)}{L^2} = 0$

Given $r(0) = K, r(x) = 0$

$$D^2 - \frac{1}{L^2} = 0$$

$$D = \pm \frac{1}{L}$$

$$r(x) = C_1 e^{-\frac{x}{L}} + C_2 e^{\frac{x}{L}}$$


$$r(0) = C_1 + C_2 = K \quad \dots (1)$$

$$r(x) = C_1 e^{-\frac{x}{L}} + C_2 e^{\frac{x}{L}} = 0$$

It is possible when $C_1 = 0$

Hence, $r(x) = C_2 e^{\frac{x}{L}} = K e^{-\frac{x}{L}}$

4. (A) The given two-port network

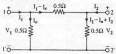

From given circuit

$$V_1 = 0.5 I_2 \quad \dots (1)$$

and $V_1 = (I_1 - I_1') 0.5 + V_2 \quad \dots (2)$

and $V_2 = (I_1 - I_1' + I_2) 0.5 \quad \dots (3)$

From equation (1) and (2)

$$V_1 = \left(I_1 - \frac{V_1}{0.5} \right) 0.5 + V_2$$

or $V_1 - 0.5 I_1 + V_1 - V_2 = 0$

or $0.5 I_1 = 2V_1 - V_2$

or $I_1 = 4V_1 - 2V_2 \quad \dots (4)$

On comparing equation (iv) with the standard equation of Y-parameter i.e. short circuit admittance parameter matrix,

$$I_1 = Y_{11}V_1 + Y_{12}V_2, \text{ we get}$$

$$Y_{11} = 4, Y_{12} = -2$$

From the given options we conclude that there is no need to solve further because these parameters are given in option (A) only.

5. (D)



$$\frac{1}{Z} = \frac{1}{sL} + \frac{1}{R} + sC$$

$$\frac{1}{Z} = \frac{s^2LCR + LS + R}{RSL}$$

$$Z(s) = \frac{RSL}{RLC \left[s^2 + \frac{1}{RC}s + \frac{1}{LC} \right]} = \frac{s}{C \left[s^2 + \frac{1}{RC}s + \frac{1}{LC} \right]}$$

$$\text{Bandwidth} = \frac{1}{RC}$$

(i) When R increase BW decrease

(ii) BW, not depend upon L


at resonance input impedance is a real quantity.

6. (B) At room temperature

$$F_{av} = 1350 \text{ cm}^2/\text{V} \cdot \text{s}$$

7. (B) Thin gate oxide in a CMOS process is preferably grown using dry oxidation.

8. (B)

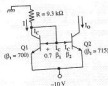

$$9.3I_e - 0.7 - 10 = 0$$

$$I_e = 1 \text{ mA}$$

$$I_e = \frac{I_{c1}}{\beta_1} + \frac{I_{c2}}{\beta_2} + I_e = 1$$

$$\frac{I_{c1}}{\beta_1} = \frac{I_{c2}}{\beta_2}$$

$$I_{c1} = \frac{\beta_1}{\beta_2} I_{c2}$$

$$I_e = \frac{I_{c1}}{\beta_1} + \frac{I_{c2}}{\beta_2} + \frac{\beta_1}{\beta_2} I_{c2}$$

$$I_{c1} = \frac{\beta_2}{1 + \beta_1 + \beta_2} \cdot 2 \cdot \beta_1 \cdot \Delta B$$

$$I_{c1} = \frac{715}{702} \cdot 2 \text{ mA}$$

9. (A)

$$R_i = r_{\pi} + (1 + \beta)R_E$$

So, input resistance R_i increase with R_E and gain

$$A_v = -\frac{R_C}{R_E} \text{ gain decrease with } R_E$$




10. (A)



$$\frac{V_i - 0}{R_1} = \frac{0 - V_o}{R_2}$$

$$V_o = -\frac{R_2}{R_1} V_i$$

11. (D)

   

P-4, Q-2, R-3, S-1.

12. (D)



Applying hit and trail method

● When $A = 1, B = 1, C = 0$

then $Y_1 = 0, Y_2 = 1, C = 0$

We know that output of EX-OR gate will be high only when the even number of inputs are high i.e. 1. Since, here the odd number of inputs are high therefore $F = 0$.

● When $A = 1, B = 0, C = 0$

then $Y_1 = 1, Y_2 = 0, C = 0$

Since, here the odd number of inputs are high therefore $F = 0$.

● When $A = 0, B = 1, C = 0$

then $Y_1 = 1, Y_2 = 0, C = 0$

Again, $F = 0$


- When $A = 0, B = 0, C = 1$

then $Y_1 = 0, Y_2 = 1, C = 1$

Since, here the even number of inputs are high, therefore $F = 1$.

Hence, alternative (D) is the correct choice.

13. (B) The given circuit

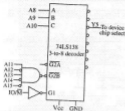

From figure we can write

$$\underbrace{A_{11} A_{12} A_{13} A_{14} A_{15}}_{\text{Applied inputs in order to make the chip enable}} \quad C \quad B \quad A$$

From the given circuit we conclude that in order to make the chip enable the output of the five inputs NAND gate must be zero. Therefore in order to make the output of NAND gate zero all the inputs should be high.

Thus, A_{11} should be high i.e. 1

A_{12} should be low i.e. 0

A_{13} should be high i.e. 1

A_{14} should be low i.e. 0

A_{15} should be low i.e. 0

Also in order to get output at pin no. 5 in a 3 to 8 decoder the inputs

CBA must be 101 i.e. 5 in decimal.

Therefore, range can be calculated as follows—

Min.

A_{11}	A_{12}	A_{13}	A_{14}	A_{15}	A_{11}	A_{12}	A_{13}	A_{14}	A_{15}	A_7	A_6	A_5	A_4	A_3	A_2	A_1	A_0
0	0	1	0	1	1	1	0	1	X	X	X	X	X	X	X	X	X
0	0	1	0	1	1	1	0	1	0	0	0	0	0	0	0	0	0
2H				0H				0H				0H					

So, minimum value = 2000 H

Max. $\frac{0}{2H} \frac{0}{12H} \frac{1}{12H} \frac{1}{12H} \frac{1}{12H} \frac{1}{12H} \frac{1}{12H} \frac{1}{12H}$

So, maximum value = 2 DFFH.

Therefore, the range $\rightarrow 2000 - 2 DFF$.

14. (A) $X(z) = 5z^2 + 4z^{-1} + 3 \quad 0 < |z| < \infty$

$x(n) = 5\delta(n+2) + 3\delta(n) + 4\delta(n-1)$

15. (C) $\xrightarrow{h_1(n)} \xrightarrow{h_2(n)}$

$h_1[n] = \delta(n-1) \quad h_2[n] = \delta(n-2)$


output = $h_1[n] * h_2[n]$

= $\delta(n-1) * \delta(n-2)$

= $\delta(n-2-1) = \delta(n-3)$

16. (C) For an N -point FFT algorithm with $N = 2^m$, in place computation requires storage of only $2N$ node data.

17. (B) The given system

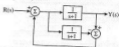

The given system can be easily solve by using signal flow graph as shown below



From above figure

$$\frac{Y(s)}{R(s)} = \frac{1}{s+1} \left[1 - 0 \right] \left[1 - \left[\frac{1}{s+1} - \frac{1}{s+1} \right] \right]$$

or $\frac{Y(s)}{R(s)} = \frac{1}{s+1}$

Hence, alternative (B) is the correct choice.

18. (B) $\frac{Y(s)}{X(s)} = \frac{s}{s+p} \quad \text{output } y(t) = \cos\left(2t - \frac{\pi}{3}\right)$

input $x(t) = P \cos\left(2t - \frac{\pi}{3}\right)$

$Y(t) = \frac{1}{2} \cos 2t + \frac{\sqrt{3}}{2} \sin 2t$

$Y(s) = \frac{s}{2(s^2+4)} + \frac{\sqrt{3}}{2} \frac{2}{s^2+4}$

$Y(s) = \frac{s+2\sqrt{3}}{2(s^2+4)}$

$x(t) = p \sin(2t)$

$X(s) = \frac{2p}{(s^2+4)}$

$\frac{Y(s)}{X(s)} = \frac{s+2\sqrt{3}}{4p} = \frac{s}{s+p}$

$(s+2\sqrt{3})(s+p) = 4sp$

$s^2 + 2\sqrt{3}s + ps + 2\sqrt{3}p = 4sp$

Equating coefficient both side of s .

$2\sqrt{3} + p = 4p$

$3p = 2\sqrt{3}$

$p = \frac{2}{\sqrt{3}}$

19. (A)



$$M(x) = \frac{K \left(\frac{x}{0.1} + 1 \right)}{\left(\frac{x}{10} + 1 \right)} = \frac{K(10x + 1)}{(x + 1)}$$

$$0 = 20 \log_{10} K$$

$$\Rightarrow K = 10^2 = J$$

$$\text{Hence } M(x) = \left[\frac{10x + 1}{0.1x + 1} \right]$$

20. (C) $m(t) = 2 \cos 2\pi f_m t$

$$x_c(t) = A_c \cos 2\pi f_c t$$

Conventional AM signal

$$x(t) = A_c [1 + \mu] \cos 2\pi f_c t$$

For without over-modulation

$$\mu < 1$$

$$x(t) = A_c \cos 2\pi f_c t + \frac{A_c \mu}{4} m(t) \cos 2\pi f_c t$$

$$x(t) = A_c \left[1 + \frac{1}{4} m(t) \right] \cos 2\pi f_c t$$

$$= A_c \left[1 + \frac{2}{4} \cos 2\pi f_m t \right] \cos 2\pi f_c t$$

$$\mu = \frac{1}{2} \text{ which is less than 1.}$$

21. (B) $x(t) = 6 \cos(2\pi \times 10^3 t) + 2 \sin(8000\pi t)$

$$+ 4 \cos(8000\pi t)$$

Average power of $x(t)$ is

$$= \frac{A^2}{2} = \frac{6^2}{2} = 18$$

22. (C)

$$[S] = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix}$$

For lossless $S_{11} = S_{22} = 0$ For reciprocal $S_{12} = S_{21}$

$$\text{Hence, } \begin{bmatrix} 0.2 \angle 0^\circ & 0.9 \angle 90^\circ \\ 0.9 \angle 90^\circ & 0.1 \angle 90^\circ \end{bmatrix}$$

not lossless but reciprocal.

23. (D) $Z_0 = 50 \Omega$, $R = 0.1 \Omega/\text{m}$

For distortionless transmission line

$$Z_0 = \sqrt{\frac{R}{G}} = 50$$

$$\frac{R}{50^2} = G$$


$$\gamma = \sqrt{RG} + j\omega\sqrt{LG} \\ = \alpha + j\beta$$

$$\alpha = \sqrt{RG} = \sqrt{\frac{R \cdot R}{50^2}} = \frac{R}{50} = \frac{0.1}{50}$$

$$\alpha = 0.002 \text{ (Np/m)}$$

24. (C) For Matched Filter

$$h(t) = S(T - t)$$

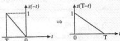25. (C) $\beta_0 E = E_0 E_0 = 4 E_0^2$

$$|E_0| = 1 \text{ v/m}$$

$$\eta = \sqrt{\frac{\mu_0}{\epsilon_0}} = \frac{120\pi}{400}$$

$$P_{\text{avg}} = \frac{1}{2} \frac{|E_0|^2}{\eta} \\ = \frac{1}{2} = \frac{1}{60\pi} = \frac{1}{120\pi}$$

$$= \frac{120\pi}{2} = 60\pi$$

26. (A)

$$\frac{1}{x} \log_a x = y$$

$$\frac{dy}{dx} = \frac{1}{x^2} - \frac{\log_a x}{x^2} \rightarrow x = a$$

$$\frac{d^2y}{dx^2} = \frac{-2}{x^3} - \left\{ \frac{1}{x^2} - \frac{2 \log_a x}{x^2} \right\} \\ = \frac{-3}{x^3} + \frac{2 \log_a x}{x^2}$$

at

$$x = a$$

$$\frac{d^2y}{dx^2} = -\frac{3}{a^3} + \frac{2}{a^2} < 0$$

Hence, y is max. at $x = a$.

27. (D) A fair coin is tossed independently 4 times probability of the event coming up head more than the event coming

$$\text{up tails} = {}^4C_2 \left(\frac{1}{2}\right)^2 \left(\frac{1}{2}\right)^2 + {}^4C_3 \left(\frac{1}{2}\right)^3 \left(\frac{1}{2}\right)^1 \\ = 4 \frac{1}{(2)^4} + 4 \frac{1}{2^4} \\ = \frac{6}{16}$$

28. (C)

$$\vec{A} = x^2\vec{a}_x + x^2\vec{a}_y, \text{ then } \oint \vec{A} \cdot d\vec{l}$$



$$\oint \vec{A} \cdot d\vec{l}$$

$$= \int_{AB} \vec{A} \cdot d\vec{l} + \int_{BC} \vec{A} \cdot d\vec{l} + \int_{CD} \vec{A} \cdot d\vec{l} + \int_{DA} \vec{A} \cdot d\vec{l}$$

$$I_1 = \int_{AB} \vec{A} \cdot d\vec{l}$$

$$y = 1 \quad dy = 0$$

$$I_1 = \int_{1/\sqrt{3}}^{2/\sqrt{3}} (x^2\vec{a}_x + x^2\vec{a}_y) \cdot (dx\vec{a}_x + 0) = \int_{1/\sqrt{3}}^{2/\sqrt{3}} x^2 dx$$

$$= \left[\frac{x^3}{3} \right]_{1/\sqrt{3}}^{2/\sqrt{3}} = \frac{1}{2} \left[\frac{8}{3} - \frac{1}{3} \right] = \frac{1}{2}$$

$$I_2 = \int_1^3 \left(\frac{2}{\sqrt{3}} y \vec{a}_x + \frac{4}{3} \vec{a}_y \right) \cdot (0 + dy\vec{a}_y) = \frac{4}{3} \int_1^3 dy = \frac{4}{3} \cdot 2 = \frac{8}{3}$$

$$I_3 = \int_{2/\sqrt{3}}^{1/\sqrt{3}} (x^2 \cdot 3\vec{a}_x + x^2\vec{a}_y) \cdot (-dx\vec{a}_x + 0) = 3 \int_{2/\sqrt{3}}^{1/\sqrt{3}} x^2 dx$$

$$= 3 \left[\frac{x^3}{3} \right]_{2/\sqrt{3}}^{1/\sqrt{3}} = -\frac{3}{2} \left[\frac{1}{3} - \frac{8}{3} \right] = -\frac{3}{2}$$

$$I_4 = \int_3^1 \left(y \frac{1}{\sqrt{3}} \vec{a}_x + \frac{1}{3} \vec{a}_y \right) \cdot (dx\vec{a}_x + dy\vec{a}_y) = \frac{1}{3} \int_3^1 dy = -\frac{2}{3}$$

Hence $I = \frac{1}{2} + \frac{8}{3} - \frac{3}{2} - \frac{2}{3} = \frac{2 + 16 - 9 - 4}{6} = \frac{19 - 13}{6} = \frac{6}{6} = 1$

29. (C) Given complex function

$$X(z) = \frac{1-2z}{z(z-1)(z-2)}$$

The poles are located at $z = 0, 1, 2$.● Residue at pole $z = 0$ is

$$f(z) \cdot z \Big|_{z=0}$$

$$\text{or } \frac{(1-2z)}{z(z-1)(z-2)} \Big|_{z=0}$$

$$\text{or } \frac{(1-2 \cdot 0)}{(0-1)(0-2)} = \frac{1}{2}$$

● Residue at pole $z = 1$ is

$$= f(z) \cdot (z-1) \Big|_{z=1}$$

$$= \frac{(1-2z)(z-1)}{z(z-1)(z-2)} \Big|_{z=1}$$

$$= \frac{1-2}{1(1-2)} = \frac{-1}{-1} = 1$$

● Residue at pole $z = 2$ is

$$= f(z) \cdot (z-2) \Big|_{z=2}$$

$$= \frac{(1-2z)(z-2)}{z(z-1)(z-2)} \Big|_{z=2}$$

$$= \frac{(1-2 \cdot 2)}{2(2-1)} = \frac{-3}{2}$$

$$= -\frac{3}{2}$$

Hence alternative (C) is the correct choice.

30. (C)


$$31. \text{ (D) } f(s) = L^{-1} \left[\frac{3s+1}{s^3+4s^2+(K-3)s} \right]$$

$$f(s) = L^{-1} \left[\frac{3s+1}{s(s^2+4s+K-3)} \right]$$



$$\lim_{s \rightarrow 0} sf(s) = \lim_{s \rightarrow 0} sF(s) = \lim_{s \rightarrow 0} \frac{3s+1}{s^2+4s^2+K-3} = 1$$

$$\frac{1}{K-3} = 1 \Rightarrow K-3=1 \Rightarrow K=4$$

32. (A)

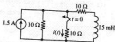Case I : $t = 0$

$$i(0^+) = \frac{1.5}{20} = 0.75 \text{ amp}$$

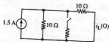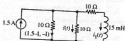Case II : for $t > 0^+$ 

$$10i_1(t) + 15 \times 10^{-3} \frac{d}{dt} i_1(t) - 10i_2(t) = 0 \quad \dots(4)$$

$$10i_1(t) - 10(1.5 - i_1 - i_2) = 0$$

$$20i_1(t) + i_2(t) = 1.5$$

$$i_2(t) = 1.5 - 2i_1(t) \quad \dots(5)$$

$$\frac{d i_1(t)}{d t} = -2 \frac{d i_1(t)}{d t} \quad \dots(6)$$

$$15 - 20i_1(t) - 15 \times 10^{-3} \times 2 \frac{d i_1(t)}{d t} - 10i_2(t) = 0$$

$$\frac{d i_1(t)}{d t} + 1000 i_1(t) = 500$$

$$I.F. = e^{\int 1000 dt} = e^{1000t}$$

$$i_1(t) \cdot e^{1000t} = \int e^{1000t} \cdot 500 dt + c$$

$$i_1(t) = \frac{1}{2} + ce^{-1000t}$$

$$i_1(0) = 1.5 - 2 \left\{ \frac{1}{2} + ce^{-1000 \cdot 0} \right\}$$

$$i_1(0) = 0.5 - 2c = 1000^{-1}$$

$$c = -0.125$$

$$0.75 = 0.5 - 2c$$


$$c = -0.125$$

$$i_1(t) = 0.5 - 0.125 e^{-1000t}$$

at

Hence,

33. (A)

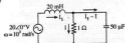

$$X_L = \omega L = 10^3 \times 20 \times 10^{-3} = 20 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{50 \times 10^{-6} \times 10^3} = \frac{1000}{50} = 20 \Omega$$

$$-20 + j20 I_1 + 1 = 0$$

$$-j20 (I_1 - I_2) - 1 = 0$$

$$20 j I_1 + 1 (20 j + 1) = 0$$

$$I_1 = -\frac{(1 - 20 j) 1}{20 j}$$

$$-20 - (1 - 20 j) 1 + 1 = 0$$

$$20 j I_1 = +20$$

$$I_1 = +\frac{1}{j} = -j$$

$$I_1 = -j \text{ amp}$$

34. (A)



$$-10 + 3(3 + 1) + 2(2 + 1) = 0$$

$$5 + 2(3) = 5$$

$$1 = 0$$

Power deliver by $10V = VI = V \times 0 = 0 \text{ watt}$

35. (B)

p^{++}	n^{+}	n
N_B	N_B	N_C

The emitter injection efficiency of the BJT will be close to unity, if $N_C \gg N_B$ and $N_B \gg N_C$.


36. (C) p-n junction 1 $N_A = N_B = 10^{14} \text{ cm}^{-3}$

p-n junction 2 $N_A = N_C = 10^{20} \text{ cm}^{-3}$

Reverse Breakdown voltate = $\frac{1}{N}$ and depletion capacitance $\propto N$.

Hence, reverse breakdown voltage is lower and depletion capacitance is higher.

37. (D)

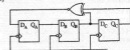

$$D_A = Q_B Q_C + \bar{Q}_B \bar{Q}_C, D_B = Q_A, D_C = Q_B$$

Q_A	Q_B	Q_C
0	0	0
1	0	0
1	1	0
0	1	1
1	0	1

$$Q_A = 01101 \dots$$

38. (B)



Applying KCL at node (1)

$$\frac{V_1 - 0}{R} + \frac{20}{4R} = \frac{0 - V_0}{R}$$

$$V_1 + 5 = -V_0$$


If $V_1 = -5$ Diode D_2 and D_1 cut-off

and $V_0 = 0$

and at $V_1 = -10$

$\rightarrow V_0 = 5 \text{ volt}$

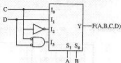Hence, alternative B is the correct choice.



AB	00	01	11	10	
00			1	1	I_4
01		1	1		I_3
11	1				I_2
10	1	1			I_1

Hence $F(ABCD) = \sum m(2, 3, 5, 7, 8, 9, 12)$.

40. (C) Given program


3000 MVI A, 45 H : A = 45 H i.e.

0	1	0	0	0	1	0	1
---	---	---	---	---	---	---	---

 3002 MOV B, A : B = 45 H i.e.

0	1	0	0	0	1	0	1
---	---	---	---	---	---	---	---

  3003 STC : Set carry i.e. $cy = 1$
 3004 CMC : Complement carry i.e. $cy = 0$
 3005 RAR : Rotate Accumulator Right through carry



3006 XRAB : X-OR-ing of content of B with Accumulator

and save the result in accumulator i.e.

$$\begin{array}{r} A = 00100010 \\ B = 01000101 \\ \hline \text{XOR B} = 01100111 \end{array}$$

Content of A =

Therefore, A = 67H

Hence alternative (C) is the correct choice.

41. (B) LTI system

$$\frac{d^2y(t)}{dt^2} + 4\frac{dy(t)}{dt} + 3y(t) = 2\frac{dx(t)}{dt} + 4x(t)$$

zero initial conditions.

Taking Laplas both side

$$s^2Y(s) + 4sY(s) + 3Y(s) = 2sX(s) + 4X(s)$$

$$Y(s)(s^2 + 4s + 3) = X(s)(2s + 4)$$

$$\frac{Y(s)}{X(s)} = \frac{2(s+2)}{(s^2 + 4s + 3)}$$

$$X(s) = \frac{1}{(s+2)}$$

Hence

$$\begin{aligned} Y(s) &= \frac{2(s+2)}{(s^2 + 4s + 3)(s+2)} \cdot \frac{1}{(s+2)} \\ &= \frac{2}{s^2 + 4s + 3} \end{aligned}$$

$$Y(s) = \frac{1}{s+1} - \frac{1}{s+3}$$

$$y(t) = (e^{-t} - e^{-3t}) u(t)$$

42. (A)

$$\begin{aligned} H(z) &= \frac{z - \frac{3}{4}z^{-1}}{1 - \frac{3}{4}z^{-1} - \frac{1}{8}z^{-2}} \\ &= \frac{2z - \frac{3}{4}}{z^2 - \frac{3}{4}z + \frac{1}{8}} \\ &= \frac{2z - \frac{3}{4}}{8z^2 - 6z + 1} \end{aligned}$$

Characteristic eq.

$$8z^2 - 6z + 1 = 0$$

$$8z^2 - 4z - 2z + 1 = 0$$

$$4z(2z - 1) - (2z - 1) = 0$$

$$z = \frac{1}{2}, \frac{1}{4}$$

and $(2z - 1)(4z - 1) > 0$



Stable and causal

$$|z| > \frac{1}{2}$$

$$|z| < \frac{1}{4}$$

and all pole lie between unit circle.

43. (C) $x(t) = \frac{\sin 500 \pi t}{\pi t} * \frac{\sin 700 \pi t}{\pi t}$

max. freq. = $\frac{1200}{2}$ Hz = 600 Hz

$$f_s = 2f_m = 600 \times 2 = 1200 \text{ Hz}$$

44. (D)



$$G'(s) = G(s) + G_c(s)$$

$$G(s) = \frac{1}{s^2 + 3s + 2}$$

- H (A)

$$G_c(s) = \frac{s+1}{s+2}$$

$$\begin{aligned} K_p &= \lim_{s \rightarrow 0} [G(s) + G_c(s)] \\ &= \frac{1}{2} + \frac{1}{2} = 1 \end{aligned}$$

$$e_{ss} = \frac{1}{1+1} = \frac{1}{2}$$

- (B)

$$G_c(s) = \frac{s+2}{s+1}$$

$$e_{ss} = \frac{1}{3-1}$$

$$(C) \quad G_c(s) = \frac{(s+1)(s+4)}{(s+2)(s+3)}$$


$$e_{ss} = \frac{1}{1 + \frac{1}{2} + \frac{2}{3}} = \frac{6}{13}$$

$$(D) \quad G_c(s) = 1 + \frac{2}{s} + 3s$$

$$e_{ss} = \frac{1}{1 + \infty} = 0$$

Hence minimum error gives D.

45. (D)

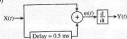

Given PSD input $S_X(f) > 0 \forall f$

$$\tau = 0.3 \text{ ms}$$

$$m(s) = x(s) + e^{-s\tau}$$

$$M(s) = X(s) [1 + e^{-s\tau}]$$

$$Y(s) = SM(s)$$

$$\frac{Y(s)}{X(s)} = j\omega [1 + e^{-j\omega\tau}]$$

$$H(j\omega)$$

$$H(j\omega) = j\omega [1 + \cos \omega\tau - j \sin \omega\tau]$$

$$S_Y(f) = |H(j\omega)|^2 S_X(f)$$

at $f = 0 \Rightarrow H(f) = 0$

Hence $S_Y(f) = 0$ for all f

at $f > 1 \text{ kHz} \Rightarrow |H(f)| > 0$ and $S_X(f) > 0$

Hence $S_Y(f) > 0$

$$S_Y(f) = 2\omega^2 [1 + \cos 2\pi f\tau - j \sin 2\pi f\tau]$$

given $f = n f_0, f_0 = 2 \times 10^3 \text{ kHz}$

$$S_Y(f) = 2\omega^2 = 2 \times 10^9$$

$$\left[\left[1 + \cos 2\pi \times n \times 2 \times \frac{1}{2} - j \sin 2\pi \times 2n \times \frac{1}{2} \right] \right]$$

$$S_Y(f) = 4\omega^2 10^9 [1 + \cos 2\pi n - j \sin 2\pi n]$$

for $n = \text{integer} \Rightarrow \cos 2\pi n = 1, \sin 2\pi n = 0$

and hence $S_Y(f) = 0$.

$$S_Y(f) = 2\omega^2 (2n+1) f_0$$

$$\left[\left[1 + \cos 2\pi \times (2n+1) \times \frac{1}{2} - j \sin 2\pi \times (2n+1) \times \frac{1}{2} \right] \right]$$

for every $n \Rightarrow \cos \pi(2n+1) = -1, \sin \pi(2n+1) = 0$.

Hence $S_Y(f) = 0$ for every f .

46. (A) $E_1 = 24 \cos(3 \times 10^3 t - \beta^2 y) \hat{a}_z \text{ V/m}$

$$\mu = \mu_0 = 0 \text{ Wb/A-m}$$

$$a_y = a_z = a_x$$



$$H_1 = |E|_{\text{top}} \cos(3 \times 10^3 t + \beta_y) \hat{a}_y \text{ A/m}$$

$$\Gamma = \frac{H_2 - H_1}{H_2 + H_1} = \frac{\frac{120a}{3} - 120a}{\frac{120a}{3} + 120a}$$


$$\Gamma = \frac{\frac{1}{3} - 1}{\frac{1}{3} + 1} = -\frac{2}{4} = -\frac{1}{2}$$

$$H_0 = \frac{E_0}{\eta} = \frac{24}{120\pi} = \frac{2}{10\pi}$$

$$H_1 = \frac{2}{10\pi} \cdot \frac{1}{2} \cos(3 \times 10^3 t + \beta_y) \hat{a}_y$$

$$H_2 = \frac{1}{10\pi} \cos(3 \times 10^3 t + \beta_y) \hat{a}_y$$

47. (B)

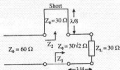

$$Z_1 = \frac{30^2}{Z_2} \text{ at } \theta = \frac{\pi}{4}$$

$$= \frac{(30\sqrt{2})^2}{30} = 60 \Omega$$

$$Z_2 = Z_0 \left[\frac{Z_1 + Z_2 \tan \beta l}{Z_0 + j Z_1 \tan \beta l} \right], Z_2 = 0$$

$$= j Z_0 \tan \beta l$$

$$\beta l = \frac{2\pi}{\lambda} \cdot \frac{\pi}{8} = \frac{\pi}{4}$$

$$Z_1 = j Z_0 = 30 j$$

$$Z = 60 + 30 j$$


$$|\Gamma| = \left| \frac{Z_L - Z_0}{Z_L + Z_0} \right| = \left| \frac{60 + 30j - 60}{60 + 30j + 60} \right|$$

$$|\Gamma| = \frac{30 j}{120 + 30 j} = \frac{1}{(\sqrt{17})}$$

$$VSWR = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + \frac{1}{\sqrt{17}}}{1 - \frac{1}{\sqrt{17}}}$$

$$VSWR = 1.64$$

42. (B)

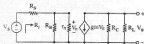

$$R_1 = R_A + R_B \parallel R_C$$


$$\text{or } R_1 = 1 + \frac{93 \times 0.250}{93 + 0.250} = 1.298 \Omega$$

$$49. (B) \quad f = \frac{1}{2\pi(R_C + R_L)C_2}$$

$$\text{or } f = \frac{1}{2\pi(0.25 + 1) \times 4.7 \times 10^{-6}}$$

$$\text{or } f = 27.1 \text{ Hz}$$

50. (D)

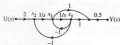

$$\dot{x}_2 = -x_1 + 2x(t)$$

$$\dot{x}_1 = -x_1 + x_2$$

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} -1 & 1 \\ -1 & 0 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 \\ 2 \end{bmatrix} u(t)$$

$$y(t) = 0.5 x_1 + 0.5 x_2$$

$$y(t) = [0.5 \quad 0.5] x(t)$$

$$51. (C) \quad M_1 = \frac{2}{s} \cdot \frac{1}{s} \cdot 0.5 = \frac{1}{s^2}$$

$$M_2 = \frac{2}{s} \cdot 1 \cdot 0.5 = \frac{1}{s}$$

$$L_{11} = -\frac{1}{s_2} L_{12} = -\frac{1}{s}$$

$$M = \frac{\frac{1}{s^2} + \frac{1}{s}}{1 + \frac{1}{s^2} + \frac{1}{s}} = \frac{s+1}{s^2+s+1}$$

52. (B) Electric field at $x = 0.5 \mu\text{m}$

$$E = 5 \text{ kV/cm}$$

53. (B) $J = qn\mu E$ $n = N_D = 10^{14} \text{ cm}^{-3}$

$$= 1.6 \times 10^{19} \times 10^{14} \times 1350 \times 5 \times 10^2$$

$$J = 1.08 \times 10^4 \text{ A/cm}^2$$

54. (B) Given $S_{av}(f) = \frac{N_0}{2} = 10^{-20} \text{ W/Hz}$

Low pass filter is ideal with unity gain

$$f_c = 1 \text{ MHz} = 1 \times 10^6 \text{ Hz}$$

The power is given by

$$= 2 S_{av}(f_c)$$

$$= 2 \times \frac{N_0}{2} \times f_c$$

$$= 2 \times 10^{-20} \times 1 \times 10^6$$

$$= 2 \times 10^{-14} \text{ watts}$$

$$\text{Variance} = \frac{2}{\alpha^2} = \text{Power}$$

(since mean is zero given)

$$\text{So, } \frac{2}{\alpha^2} = 2 \times 10^{-14}$$

$$\text{or, } \alpha = 10^7$$

Hence, alternative (B) is the correct.

55. (D) 56. (B) 57. (A) 58. (D) 59. (B) 60. (D)

61. (C) 62. (A) 63. (D) 64. (B) 65. (B)